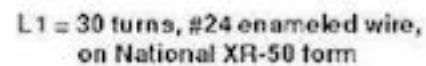


104 Ham Radio Projects for Novice and Technician
by Bert Simon, W2UUN
TAB Books, 1968

104 Ham Radio Projects for Novice and Technician
by Bert Simon, W2UUN
TAB Books, 1968



T1 = Thordarson T13R13
700 VCT
5.0 VAC
6.3 VAC

117V AC

5A

Stancor

Close this switch to transmit.

40 μ F,
450 VDC

40 μ F,
450 VDC

100K,
10W

6.3
AC
$$\sum_2 v_2$$

I could read these like a book!